

# Digital Logic Circuits 'Sequential Logic Analysis' ELEC2200

David J. Broderick  
[brodedj@auburn.edu](mailto:brodedj@auburn.edu)  
<http://www.auburn.edu/~brodedj>  
Office: Broun 360



# Sequential Analysis

- Divides into two categories
  - Given a circuit, find the state table and diagram
  - Given a state and an input sequence, what will the output sequence be?
- We'll perform both today and through the rest of the semester




# Sequential Analysis

- Use combinational analysis to write the expressions for each flip-flop input and each output.
- Use characteristics of flip-flops to construct state table
- Draw state diagram based on state table
- Use state diagram to find state/output sequence


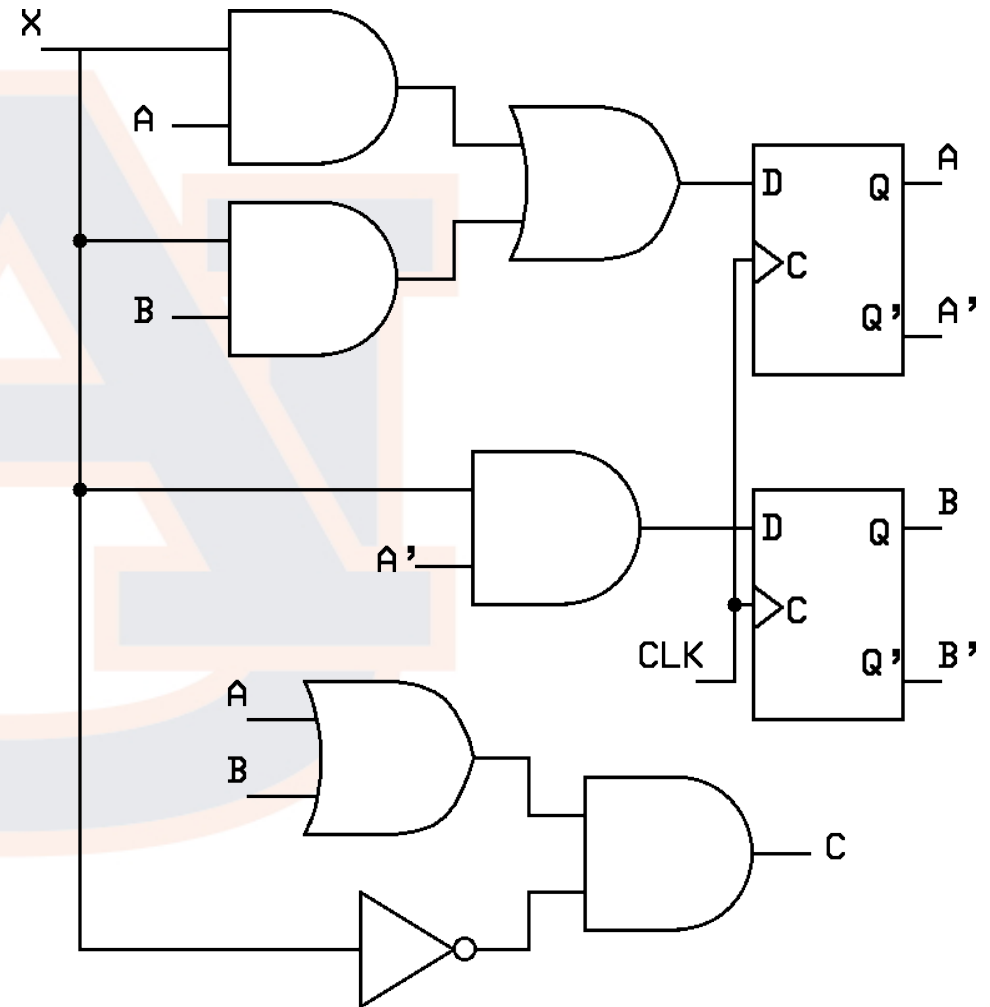
# Analysis Example

- Given this sequential logic circuit and:
  - An initial state of  $A=0, B=1$
  - An input sequence of  $X=010011$
- What will the final state be?
- What will the output sequence be?



# Analysis Example

Use combinational analysis to write the expressions for each flip-flop input and each output


- Flip-flop inputs

- $D_A = X \cdot A + X \cdot B$

- $D_B = X \cdot A'$

- Output

- $C = X' \cdot (A + B)$

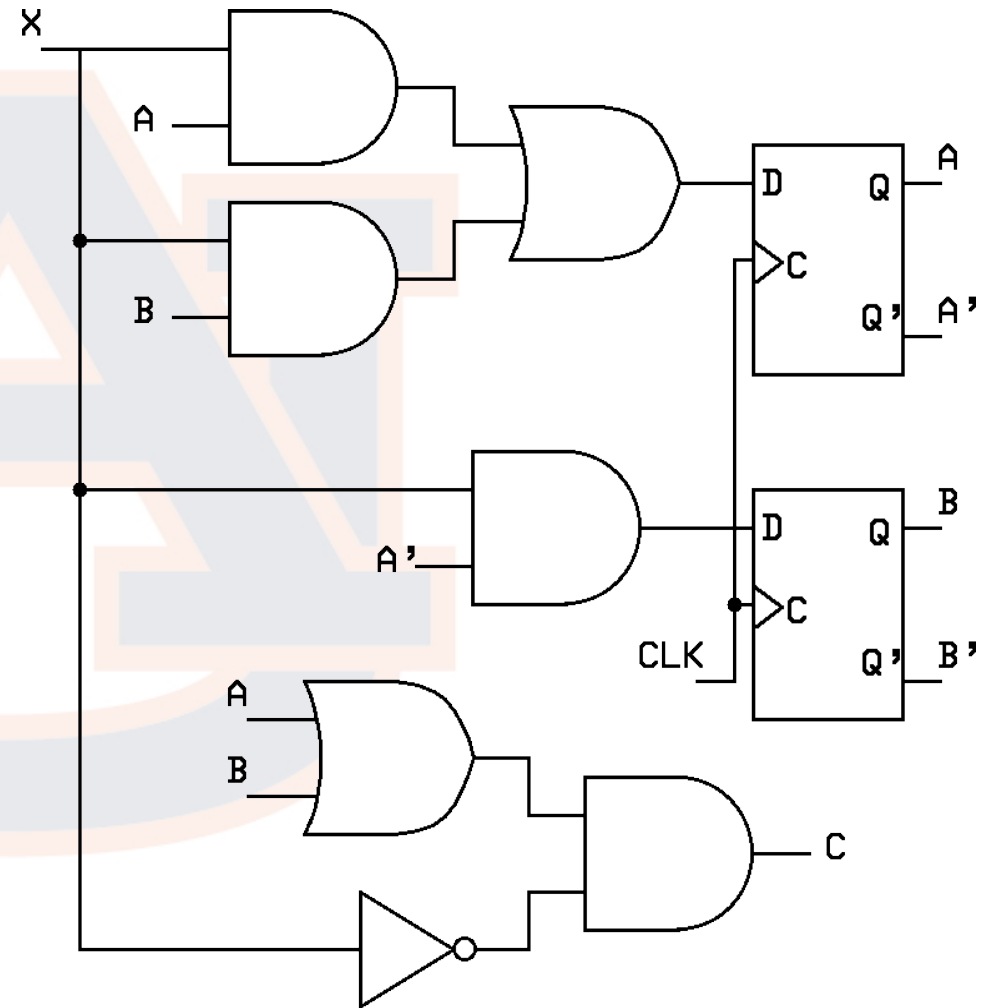

# Analysis Example


Use characteristics of flip-flops to construct state table

$$D_A = X \cdot A + X \cdot B$$

$$D_B = X \cdot A'$$

$$C = X' \cdot (A + B)$$


Input	Curr. State		Next State		Output
X	A	B	A	B	C
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

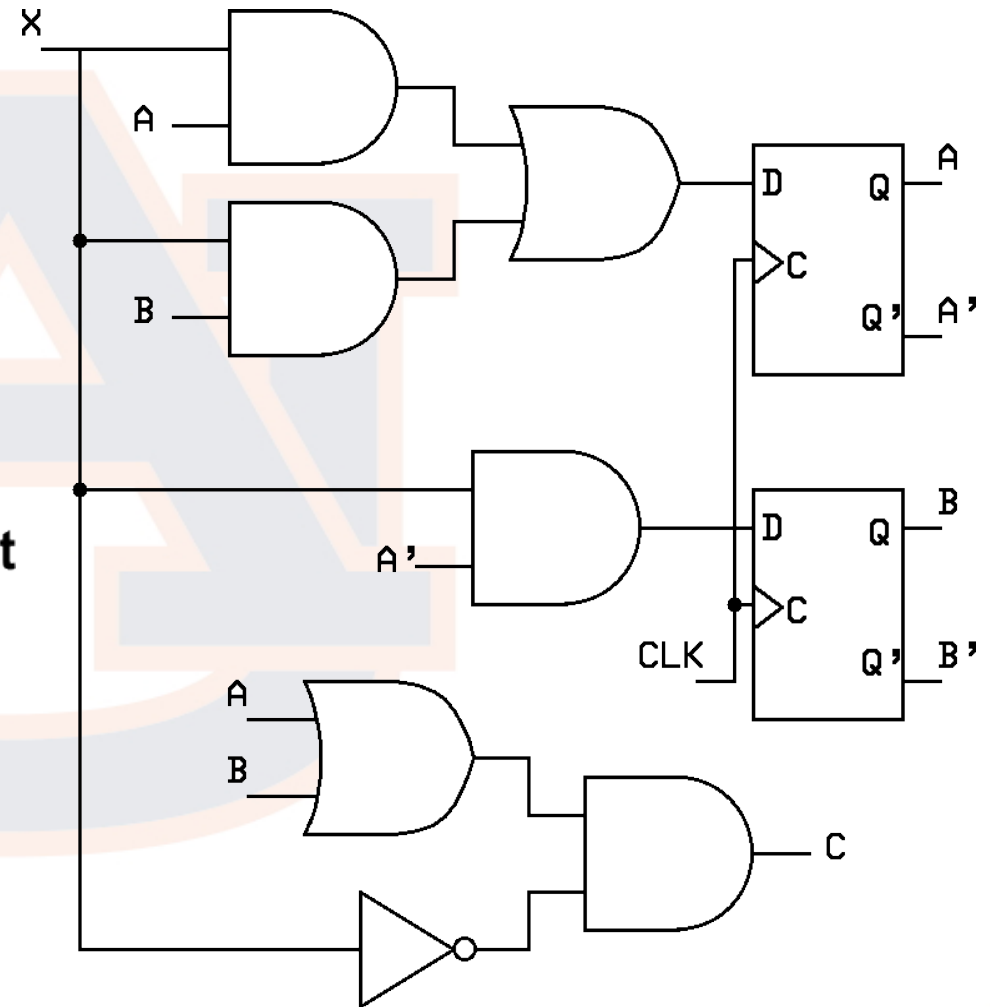

# Analysis Example

Draw state diagram  
based on state table


Input X	Curr. State		Next State		Output C
	A	B	A	B	
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

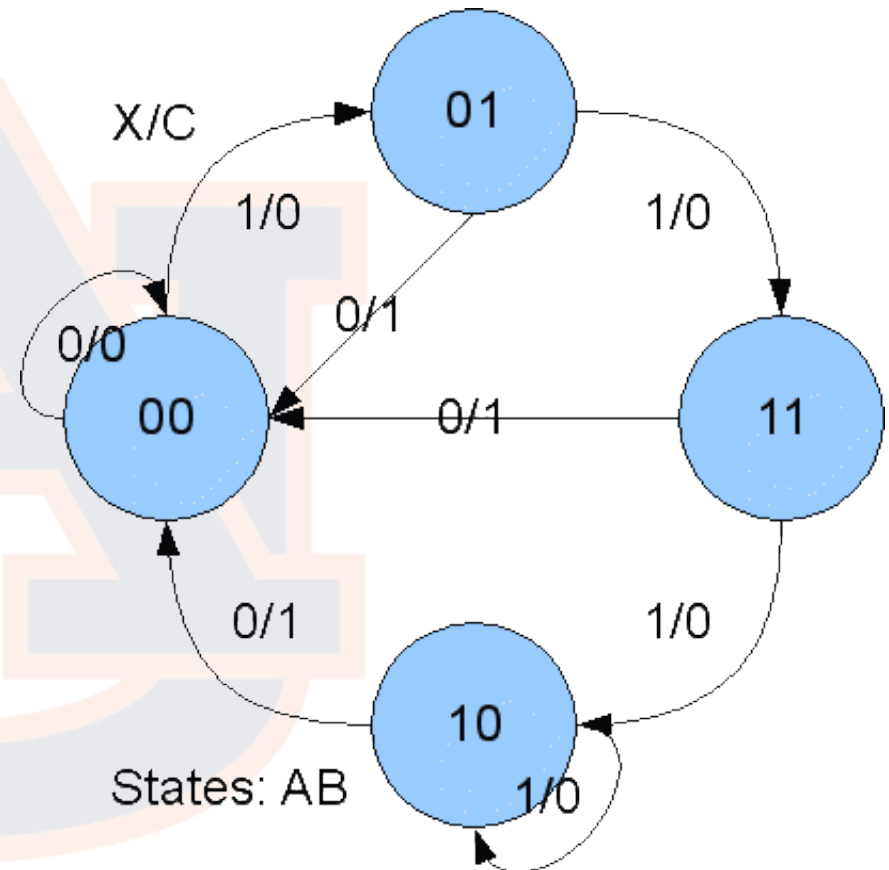
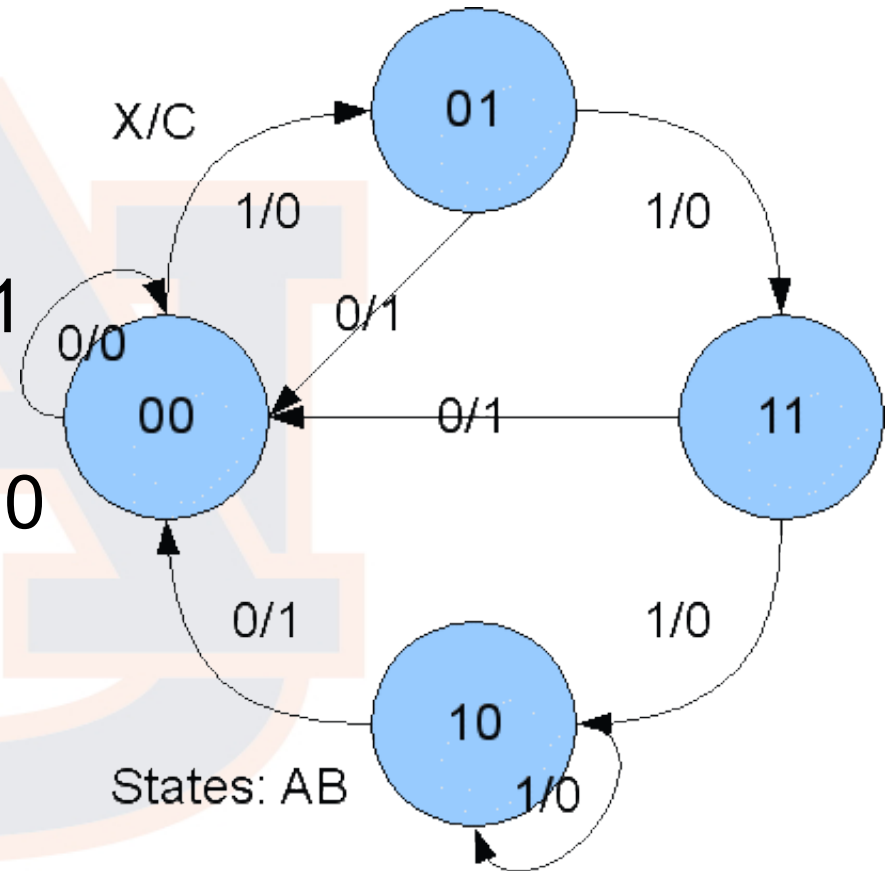
# Analysis Example

Use state diagram to find state/output sequence


- $X=010011$
- initial state of  $A=0, B=1$
- State order  
AB=01,00,01,00,00,0  
1,11
- Output  
C=1,0,1,0,0,0




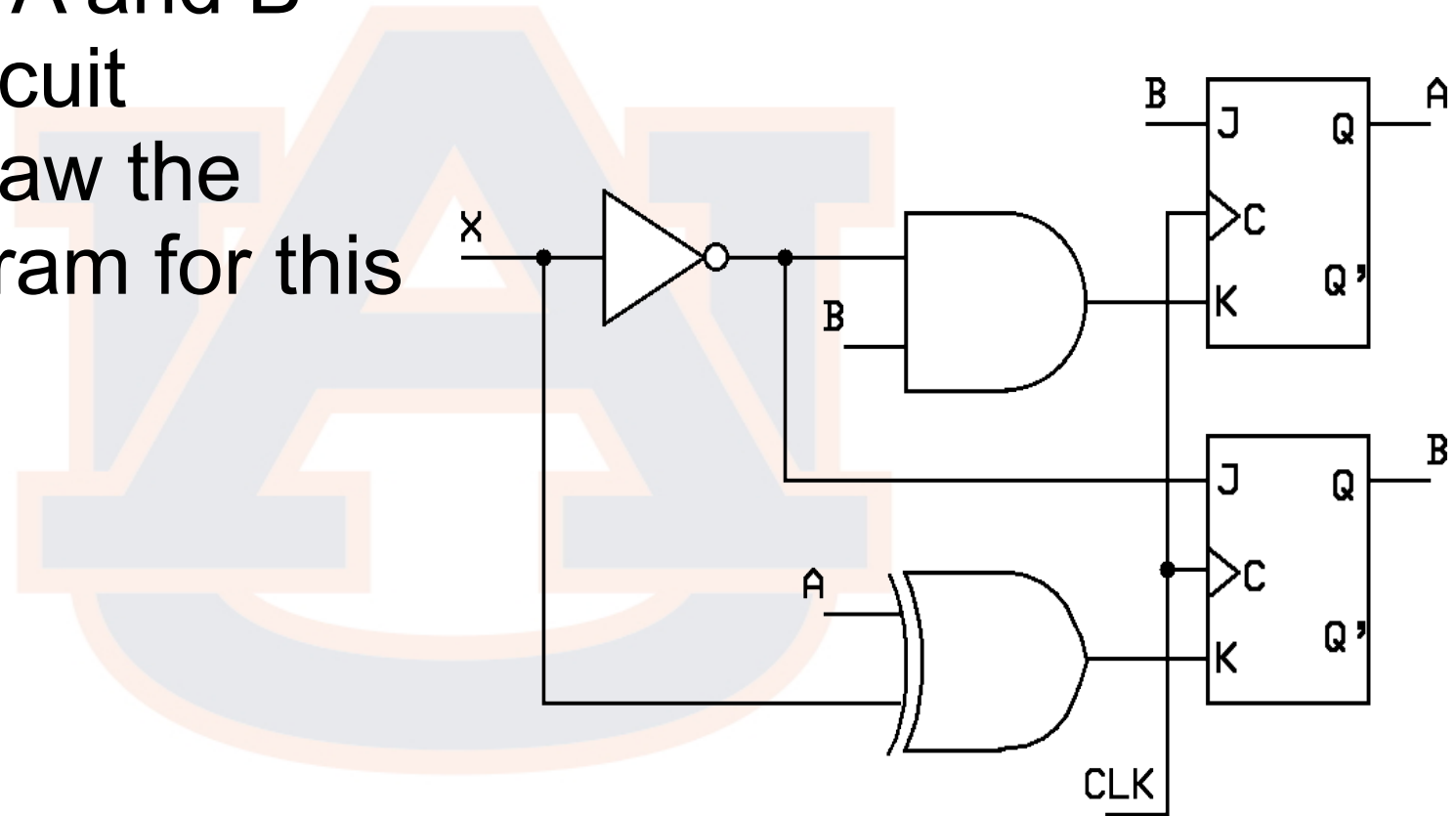
# JK Circuit Analysis


- Assuming A and B are the circuit outputs draw the state diagram for this circuit


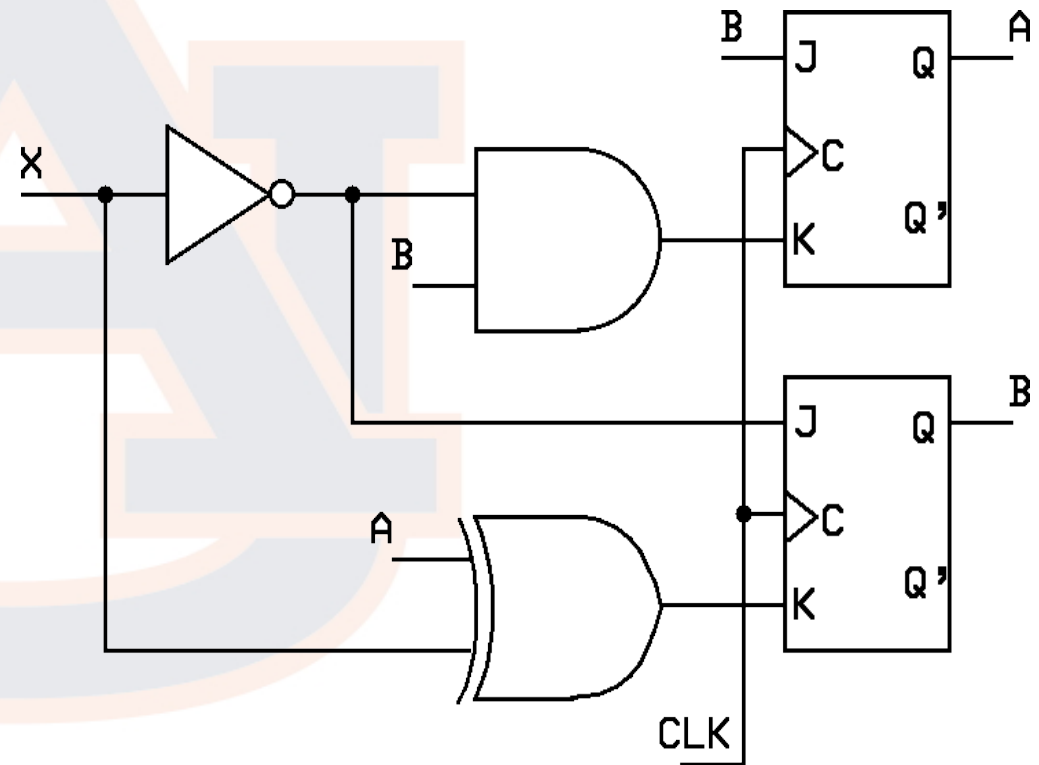
# JK Circuit Analysis

Use combinational analysis to write the expressions for each flip-flop input and each output

- Flip-flop inputs
  - $J_A = B$
  - $K_A = X' \cdot B$
  - $J_B = X'$
  - $K_B = A(+ )X$



# JK Circuit Analysis

Use characteristics of flip-flops to construct state table


$$J_A = B$$

$$K_A = X' \cdot B$$

$$J_B = X'$$

$$K_B = A(+ )X$$


Input X	Curr. State		Next State		Excitation			
	A	B	A	B	Ja	Ka	Jb	Kb
0	0	0	0	1	0	0	1	0
0	0	1	1	1	1	1	1	0
0	1	0	1	1	0	0	1	1
0	1	1	0	0	1	1	1	1
1	0	0	0	0	0	0	0	1
1	0	1	1	0	1	0	0	1
1	1	0	1	0	0	0	0	0
1	1	1	1	1	1	0	0	0

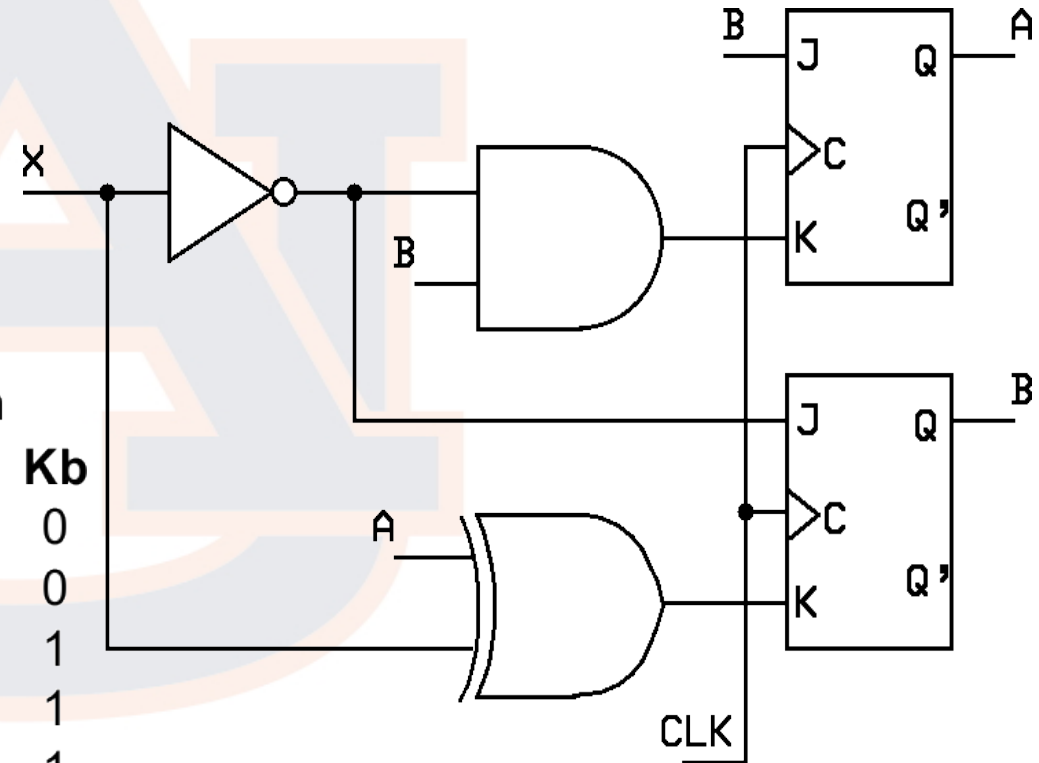

# JK Circuit Analysis


Draw state diagram based on state table

Input X	Curr. State		Next State		Excitation			
	A	B	A	B	Ja	Ka	Jb	Kb
0	0	0	0	1	0	0	1	0
0	0	1	1	1	1	1	1	0
0	1	0	1	1	0	0	1	1
0	1	1	0	0	1	1	1	1
1	0	0	0	0	0	0	0	1
1	0	1	1	0	1	0	0	1
1	1	0	1	0	0	0	0	0
1	1	1	1	1	1	0	0	0

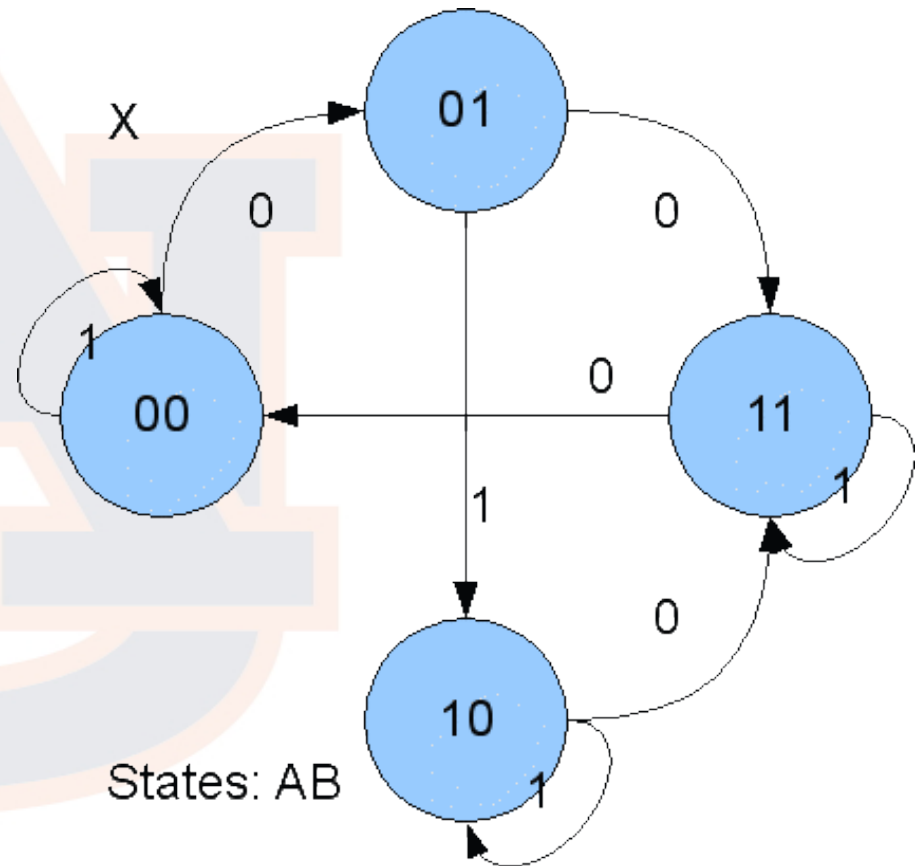
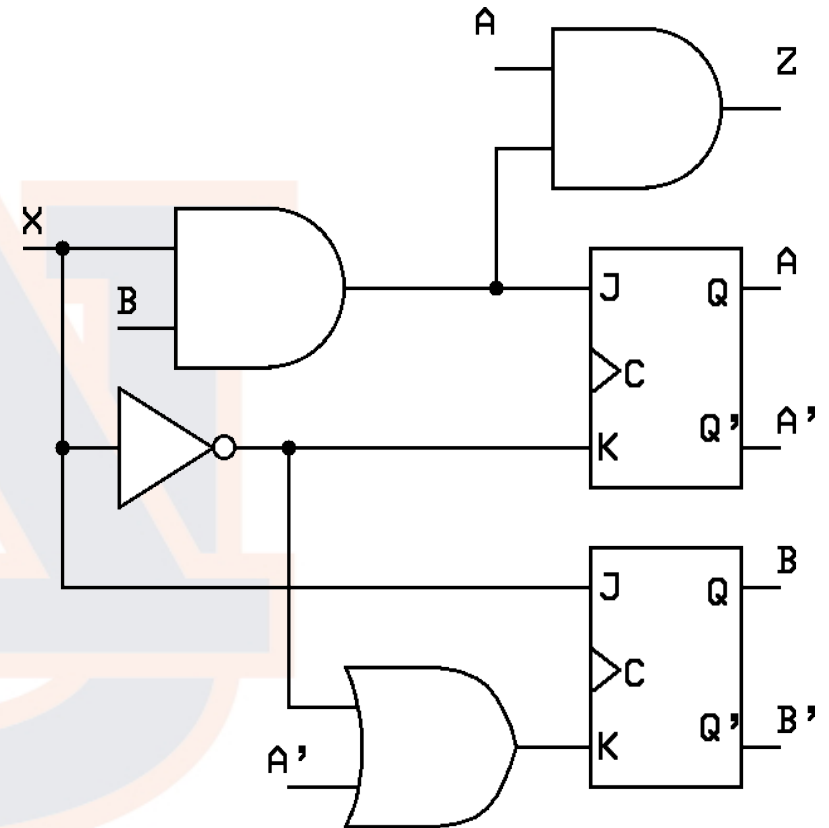
# JK Exercise

- Draw the state diagram
- Given the initial state  $A=1$  and  $B=0$  and the input  $X=1001111$ , find the output sequence



# D Exercise

- Draw the state diagram
- Given the initial state  $C=0$  and input  $A=0011$ ,  $B=0101$   
Find the sequence of states and output

